

# RADIO ELECTRONICS

BULLETIN No. 113

June, 1941

## CATHODE BYPASSING

### Derivation of Mathematical Formula

In the Radiotron Designer's Handbook (chapter 4, page 27) a formula is given for the response of a single stage due to the effect of the cathode bypass condenser. The derivation of this formula in the more convenient, explicit form is now given and the result shown to be identical with that previously obtained. For convenience, a family of curves is also given for response against frequency, with capacitance as parameter, for type 6J7-G valves operated under standard conditions.

#### Analysis

The notation to be used is as follows :

- $e_i$  = Instant. a-c. input voltage.
- $e_g$  = Instant. a-c. grid voltage with respect to cathode.
- $e_k$  = Instant. a-c voltage developed across self-bias resistor with respect to cathode.
- $e_p$  = Instant. plate voltage with respect to cathode.
- $e_o$  = Instant. effective output voltage.
- $R_K$  = Resistance of self-bias resistor.
- $C_K$  = Capacitance of cathode bypass condenser.
- $R_L$  = Effective a-c plate load resistance.
- $\mu$  = Valve amplification factor at the operating point.
- $g_m$  = Valve mutual conductance at the operating point.
- $r_p$  = Valve plate resistance at the operating point.
- $\omega$  =  $2\pi f$  rad./sec.
- $f$  = Frequency of operation (c/s.).
- $M$  = Stage amplification with self-bias resistor completely bypassed.
- $M''$  = Stage amplification with self-bias resistor incompletely bypassed.

In Fig. 1 the circuit is shown of a conventional self-biased stage, together with the instantaneous

A.C. voltages developed across the valve electrodes and associated circuits, when an instantaneous a-c input voltage  $e_i$  is applied. The plate load impedance is assumed to be non-reactive

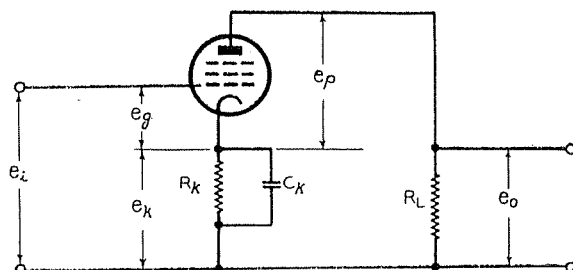


Fig. 1.

and the relative phases of all voltages referred to that of the cathode. It is then evident that

$$e_p = e_o + e_k \dots \dots \dots (1)$$


$$e_i = e_g - e_k \dots \dots \dots (2)$$

$$\text{and } e_k = e_o \cdot \frac{Z_k}{R_L} \dots \dots \dots (3)$$

where  $Z_k$  is the parallel impedance of  $R_K$  and  $C_K$  at the frequency  $\omega$  rad./sec.

(Continued overleaf, column 1.)



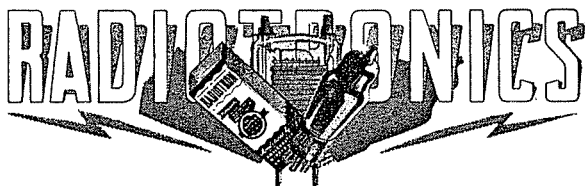

TECHNICAL BULLETIN, No. 113

JUNE, 1941

\* \* \*

## CONTENTS

|                            | Page |
|----------------------------|------|
| Cathode Bypassing          | 39   |
| Radiotron News             | 42   |
| Equivalent Type Chart      | 42   |
| Radiotronics Subscriptions | 42   |
| New Radiotron Chart        | 42   |
| Valve Data Sheets          | 42   |

\* \* \*

Radiotronics Technical Bulletins are available by annual subscription to the Head Office of the Company:

AMALGAMATED WIRELESS VALVE CO.  
PTY. LTD.

"Wireless House," 47 York Street,  
Sydney, N.S.W. (G.P.O. Box 2516 BB).

Subscriptions are accepted for the full 12 months (January-December) ONLY and preceding numbers are supplied subject to stocks being available. Subscribers are requested to remit money by Postal Note.

Subscription—two shillings (2/-) per year.

\* \* \*

Articles published in Radiotronics Technical Bulletins may be reprinted wholly or in part on the express condition that acknowledgment shall be made to the source of such material.

\* \* \*

Published by The Wireless Press for Amalgamated Wireless Valve Co. Pty. Ltd. Wholly set up and printed in Australia by The Cloister Press, 45-49 George Street, Redfern.

(Continued from page 39.)

$$\text{Since } e_p = -\mu \cdot e_g \cdot \frac{R_L + Z_k}{R_L + Z_k + r_p} \dots (4)$$

$$\therefore e_o = -\mu \cdot e_g \cdot \frac{R_L}{R_L + Z_k + r_p} \dots (5)$$

$$\text{Also, } e_i = e_g \cdot \left(1 + \frac{\mu \cdot Z_k}{R_L + Z_k + r_p}\right) \dots (6)$$

The *degenerative* stage amplification  $M''$  with the impedance  $Z_k$  in the cathode circuit is then given by—

$$M'' = \frac{e_o}{e_i} = \frac{-\mu R_L}{R_L + r_p + Z_k(\mu + 1)} \dots (7)$$

When  $Z_k \rightarrow 0$  at the frequency  $\omega$  rad./sec.,

i.e. when the self-bias resistor  $R_K$  is *completely bypassed at this frequency*, the *normal* stage amplification  $M$  is given by—

$$M = \frac{e_o}{e_g} = \frac{-\mu R_L}{R_L + r_p} \dots (8)$$

$(Z_k \rightarrow 0).$

Hence the ratio to which the stage amplification is reduced *at the frequency*  $\omega$  rad./sec. due to incomplete cathode bypassing is—

$$\frac{M''}{M} = \frac{1}{1 + \frac{\mu + 1}{R_L + r_p} \cdot Z_k} \dots (9)$$

Substituting for  $Z_k$

$$Z_k = \frac{R_k}{1 + j\omega C_k R_k} \dots (10)$$

and putting

$$\frac{\mu + 1}{R_L + r_p} = \gamma \dots (11)$$

the expression (9) becomes

$$\frac{M''}{M} = \frac{1}{1 + \gamma \cdot \frac{R_k}{1 + j\omega C_k R_k}} \dots (12)$$

of which the *modulus* is

$$\left| \frac{M''}{M} \right| = \sqrt{\frac{1 + (\omega C_k R_k)^2}{(1 + \gamma R_k)^2 + (\omega C_k R_k)^2}} \dots (13)$$

which gives *explicitly* the *exact scalar ratio* to which the voltage amplification of a stage is reduced at the frequency  $\omega$  rad./sec. due to incomplete cathode bypassing.

The *attenuation* in decibels is then—

Attenuation—

$$(db) = 20 \log \sqrt{\frac{1 + (\omega C_k R_k)^2}{(1 + \gamma R_k)^2 + (\omega C_k R_k)^2}} \dots (14)$$

In the Radiotron Designer's Handbook (Chap. 4, page 27) the formula given is

$$\left| \frac{M''}{M} \right| = \sqrt{\frac{1 + (\omega C_k R_k)^2}{(1 + a M R_k)^2 + (\omega C_k R_k)^2}} \dots (15)$$

$$\text{where } a = \frac{1}{M(R_L + r_p)} + \frac{1}{R_L} \dots (16)$$

and the other symbols are as defined in the present notation. This formula is in an implicit form but on substituting the expression (8) for  $M$  in the first term in the denominator, it is seen that—

$$aM = \frac{\mu + 1}{R_L + r_p} = \gamma$$

and the two formulae become *identical*.

In the case of *high- $\mu$  pentode valves*, generally

$$r_p \gg R_L$$


$$\& \mu \gg 1$$

so that  $\gamma \doteq g_m \dots$

and the *exact* expression (13) may be written as the more immediately applicable *approximation*—

$$\left| \frac{M''}{M} \right| = \sqrt{\frac{1 + (\omega C_k R_k)^2}{(1 + g_m R_k)^2 + (\omega C_k R_k)^2}} \dots (17)$$

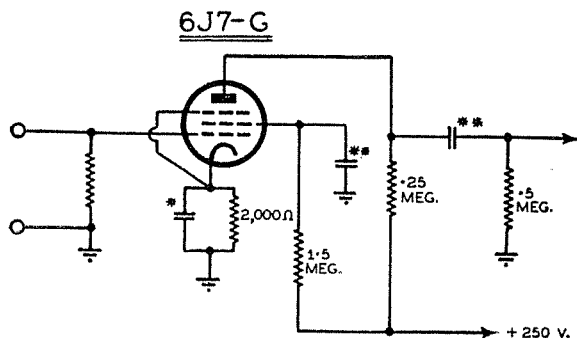which is usually sufficiently accurate for most practical purposes.



\* FOR VALUES SEE FIG. 3

\*\* ASSUMED TO HAVE NEGLECTIBLE REACTANCE

Fig. 2.

Owing to the number of independent variables involved, it is difficult to represent the formulae (13) or (16) in convenient, general graphical form. A useful set of curves, however, is obtained

by plotting a family of curves of  $C_k$  for  $\left| \frac{M''}{M} \right|$

or  $20 \log \left| \frac{M''}{M} \right|$  against  $f$  for relevant valve types, when operated under specified standard conditions.

In Fig. 3, the latter family of curves has been plotted for type 6J7-G (6C6, 1603) when operation is under the following conditions:

|            |                       |
|------------|-----------------------|
| $E_b$      | = 250 volts           |
| $R_L$ (DC) | = 0.25 megohm         |
| $R_g$      | = 0.5 megohm          |
| $R_s$      | = 1.5 megohms         |
| $R_k$      | = 2,000 ohms          |
| $g_m$      | = 750 $\mu$ mhos      |
| $r_p$      | = 4.0 megohms approx. |

The effective A.C. plate load resistance  $R_L$  is given by

$$R_L = \frac{R_L(D.C.) \times R_g}{R_L(D.C.) + R_g}$$

$$= \frac{.25 \times .5}{.25 + .5} = .167 \text{ Megohm.}$$

$$\text{and } \gamma = \frac{\mu + 1}{R_L + r_p} = \frac{g_m \cdot r_p + 1}{R_L + r_p}$$

$$= \frac{(750 \times 10^{-6})(4 \times 10^6) + 1}{.167 + 4} \mu\text{mhos}$$

$$= \frac{3001}{4.167} \mu\text{mhos}$$

$$= 720 \mu\text{mhos}$$

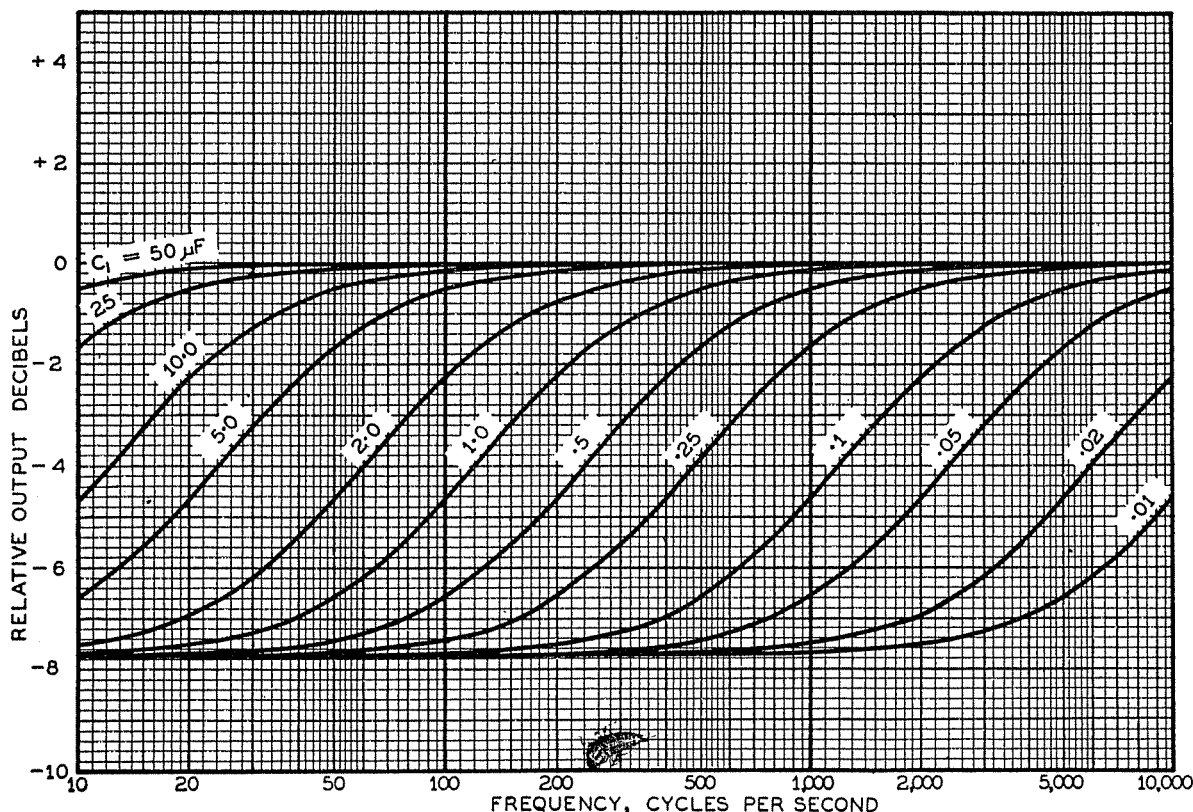


Fig. 3.